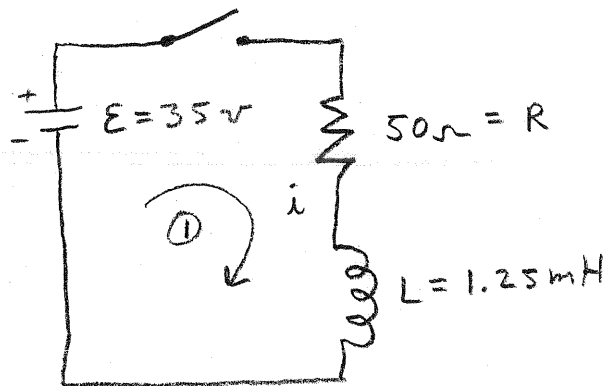


# HW 21

**30.21** A 35.0-V battery with negligible internal resistance, a 50.0-Ω resistor, and a 1.25-mH inductor with negligible resistance are all connected in series with an open switch. The switch is suddenly closed. a) How long after closing the switch will the current through the inductor reach one-half of its maximum value? b) How long after closing the switch will the energy stored in the inductor reach one-half of its maximum value?



KVL ①  $\Rightarrow \mathcal{E} - iR - L \frac{di}{dt} = 0$   
 Voltage Loop Rule

$$\Rightarrow \frac{di}{dt} = \frac{\mathcal{E}}{L} - \frac{R}{L} i \Rightarrow \frac{\left(\frac{di}{dt}\right) dt}{-\frac{R}{L} i + \frac{\mathcal{E}}{L}} = dt$$

$$\int_{i=0}^i \frac{di' L/R}{-i' + \frac{\mathcal{E}}{R}} = \int_0^t dt' \Rightarrow -\frac{L}{R} \ln\left(\frac{\frac{\mathcal{E}}{R} - i}{\frac{\mathcal{E}}{R}}\right) = t$$

$$\frac{\mathcal{E}}{R} - i = \frac{\mathcal{E}}{R} e^{-\frac{tR}{L}} \Rightarrow i = \frac{\mathcal{E}}{R} (1 - e^{-\frac{tR}{L}})$$

$$\Rightarrow i_{\max} = \frac{\mathcal{E}}{R} \quad t_{1/2} = -\frac{L}{R} \ln\left(\frac{1}{2}\right) = -\frac{1.25 \text{ mH}}{50 \Omega} \ln\left(\frac{1}{2}\right) \approx \boxed{17.3 \mu\text{s}}$$


b)  $U = \frac{1}{2} L i^2 \quad U_{\max} = \frac{1}{2} L \left(\frac{\mathcal{E}}{R}\right)^2 = \frac{1}{2} L \left(\frac{\mathcal{E}}{R}\right)^2 (1 - e^{-\frac{tR}{L}})^2$

$$U = \frac{U_{\max}}{2} \Rightarrow (1 - e^{-\frac{tR}{L}})^2 = \frac{1}{2} \Rightarrow 1 - e^{-\frac{tR}{L}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow e^{-\frac{tR}{L}} = \left(1 - \frac{1}{\sqrt{2}}\right) \Rightarrow -\frac{tR}{L} = \ln\left(1 - \frac{1}{\sqrt{2}}\right) \Rightarrow t = -\frac{L}{R} \ln\left(1 - \frac{1}{\sqrt{2}}\right)$$

$$\Rightarrow t_{1/2 \text{ Power}} = -\frac{1.25 \text{ mH}}{50 \Omega} \ln\left(1 - \frac{1}{\sqrt{2}}\right) \approx \boxed{30.7 \mu\text{s}}$$

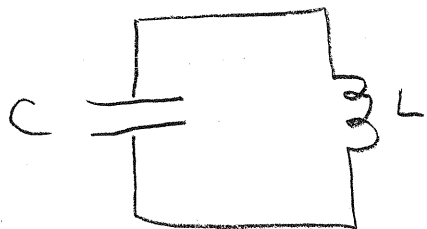30.31 When a voltmeter is placed across the plates of a capacitor, it reads 4.29 mV when the plates carry a charge of magnitude 150 nC. If the capacitor is now charged to 45.0 V and connected across a coil of negligible resistance, you observe that the current in the circuit oscillates with a period of 911  $\mu$ s. Find the capacitance of the capacitor and the inductance of the coil.



$$C = \frac{Q}{V} = \frac{150 \text{ nC}}{4.29 \text{ mV}} \left( \frac{10^{-9} \text{ m}}{10^{-3}} \right)$$


$$= \boxed{34.96 \text{ } \mu\text{C}}$$

$$\omega = \sqrt{\frac{1}{LC}} \Rightarrow T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC}$$

$$\Rightarrow LC = \left(\frac{T}{2\pi}\right)^2 \Rightarrow L = \frac{T^2}{(2\pi)^2} \frac{1}{C} = \frac{(911 \text{ } \mu\text{s})^2}{(2\pi)^2} \frac{1}{(34.96 \text{ } \mu\text{C})}$$

$$\Rightarrow L = \boxed{601 \text{ } \mu\text{H}}$$

digression

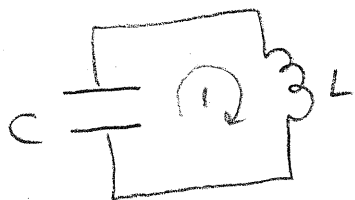


$$\text{KVL} \Rightarrow -\frac{q}{C} - L \frac{di}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} = -\frac{C}{L} q \Rightarrow \frac{d^2 i}{dt^2} = -\underbrace{\left(\frac{C}{L}\right)}_{\omega^2} i \Rightarrow \text{SHM}$$

Simple Harmonic Motion

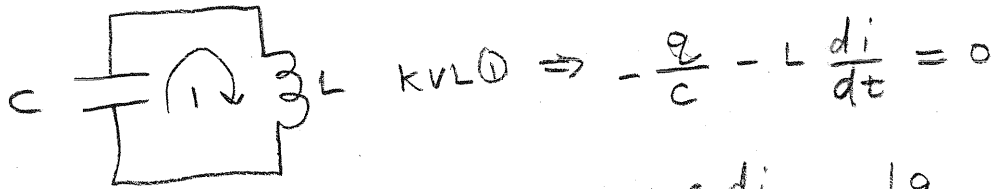30.32 In an  $L$ - $C$  circuit,  $L = 85.0$  mH and  $C = 3.20$   $\mu$ F. During the oscillations the maximum current in the inductor is  $0.850$  mA.  
 a) What is the maximum charge on the capacitor? b) What is the magnitude of the charge on the capacitor at an instant when the current in the inductor has magnitude  $0.500$  mA?



$$\Rightarrow q = -LC \frac{di}{dt} \quad |q_{\max}| = |LC| \left| \frac{di}{dt} \right|_{\max}$$

$$i = i_{\max} \sin\left(\frac{t}{\sqrt{LC}} + \phi_0\right) \quad \frac{di}{dt} = \frac{i_{\max}}{\sqrt{LC}} \cos\left(\frac{t}{\sqrt{LC}} + \phi\right)$$

$$\Rightarrow |q_{\max}| = LC \frac{i_{\max}}{\sqrt{LC}} \left| \cos\left(\frac{t}{\sqrt{LC}} + \phi\right) \right|_{\max} = \sqrt{LC} i_{\max}$$

$$= \sqrt{85 \text{ mH} (3.2 \text{ } \mu\text{F})} (10^{-3} (10^{-6}))^{1/2} \cdot 85 \text{ mA}$$

$$= \boxed{4.433 \times 10^{-7} \text{ C}}$$

$$q = LC \frac{di}{dt}$$


SHM  
 $\Rightarrow$

$$\frac{1}{2} \omega^2 i_{\max}^2 = \frac{1}{2} \omega^2 i^2 + \frac{1}{2} \left(\frac{di}{dt}\right)^2 \Rightarrow \frac{di}{dt} = \omega \sqrt{i_{\max}^2 - i^2}$$

$$\Rightarrow q = LC \omega \sqrt{i_{\max}^2 - i^2} = \sqrt{LC} \omega \sqrt{i_{\max}^2 - i^2} = q_{\max} \sqrt{1 - \left(\frac{i}{i_{\max}}\right)^2}$$

$$= (4.433 \times 10^{-7} \text{ C}) \sqrt{1 - \left(\frac{0.5}{0.85}\right)^2} = \boxed{3.585 \times 10^{-7} \text{ C}}$$

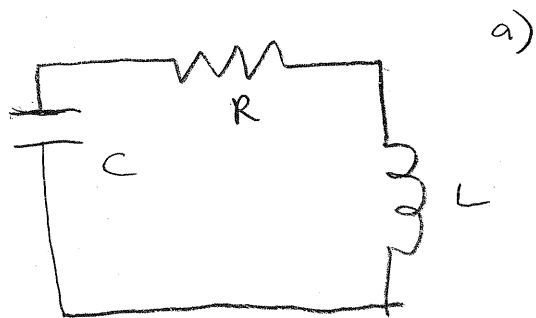30.42 An  $L$ - $R$ - $C$  circuit has  $L = 0.450$  H,  $C = 2.50 \times 10^{-5}$  F, and resistance  $R$ . a) What is the angular frequency of the circuit when  $R = 0$ ? b) What value must  $R$  have to give a 5.0% decrease in angular frequency compared to the value calculated in part (a)?



$$\omega = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{.45 \text{ H} (2.5 \times 10^{-5} \text{ F})}}$$

$$= \boxed{298.142 \frac{\text{rad}}{\text{s}}}$$

b)

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$\frac{\omega - \omega'}{\omega} = 0.05 = \frac{\sqrt{\frac{1}{LC}} - \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}{\sqrt{\frac{1}{LC}}}$$

$$= \frac{1 - \sqrt{1 - \frac{R^2 LC}{4L^2}}}{1}$$

$$\Rightarrow \sqrt{1 - \frac{R^2 C}{4L}} = 1 - 0.05$$

$$\Rightarrow 1 - \frac{R^2 C}{4L} = (.95)^2 \Rightarrow \frac{R^2 C}{4L} = 1 - (.95)^2$$

$$\Rightarrow R^2 = \frac{4L}{C} [1 - (.95)^2] = \frac{4 (.45 \text{ H})}{(2.5 \times 10^{-5} \text{ F})} [1 - (.95)^2]$$

$$\Rightarrow R \approx \boxed{83.8 \Omega}$$

30.64 In the circuit shown in Fig. 30.23, find the reading in each ammeter and voltmeter at the following times a) just after switch S is closed; b) after S has been closed a very long time.


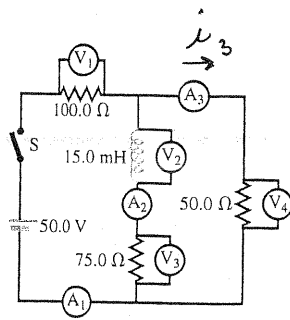


Figure 30.23 Problem 30.64.

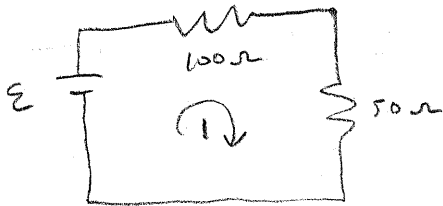a) When the switch is closed, at  $t=0$ , the inductor will act like an open circuit for an instant.



$$\text{KVL } \textcircled{1} \Rightarrow i_3 = \frac{50\text{V}}{150\Omega}$$

$$\Rightarrow i_3 = \underline{\underline{\frac{1}{3}\text{A}}}$$

$$V_1 = i_3 R_1 = \left(\frac{1}{3}\text{A}\right) 100\Omega = \underline{\underline{33.\bar{3}\text{V}}}$$

$$V_4 = i_3 R_4 = \left(\frac{1}{3}\text{A}\right) 50\Omega = \underline{\underline{16.\bar{6}\text{V}}}$$

$$V_3 = \underline{\underline{0}} \quad i_1 = i_3 = \underline{\underline{\frac{1}{3}\text{A}}}$$

$$\text{KVL } \textcircled{2} \Rightarrow \varepsilon - i_3 R_3 - V_2 = 0 \quad i_2 = \underline{\underline{0}}$$

$$\Rightarrow V_2 = \varepsilon - i_3 R_3 = 50\text{V} - 33.\bar{3}\text{V} = \underline{\underline{16.\bar{6}\text{V}}}$$

b) after  $t \rightarrow \infty$  the inductor is like a short.

$$i_1 = \frac{50\text{V}}{100\Omega + \left(\frac{75(50)}{75+50}\right)\Omega} = \underline{\underline{0.3846\text{A}}} \quad V_1 = i_1 R_1 = \underline{\underline{38.46\text{V}}}$$

$$i_2 = \frac{V_3}{R_3} = \underline{\underline{0.154\text{A}}}$$

$$V_4 = \varepsilon - V_1 = 50\text{V} - 38.4615\text{V} = \underline{\underline{11.54\text{V}}} = V_3 \Rightarrow$$

$$i_3 = i_1 - i_2 = 0.231\text{A}$$

30.68 In the circuit shown in Fig. 30.27, the capacitor is originally uncharged. The switch starts in the open position and is then flipped to position 1 for 0.500 s. It is then flipped to position 2 and left there. a) If the resistance  $r$  is very small, what is the upper limit for the amount of charge the capacitor could receive? b) Even if  $r$  is very small, how much electrical energy will be dissipated in it? c) Sketch a graph showing the reading of the ammeter as a function of time after the switch is in position 2, assuming that  $r$  is small.


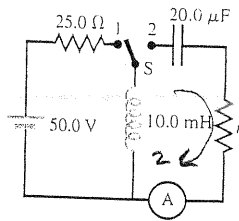


Figure 30.27 Problem 30.68.

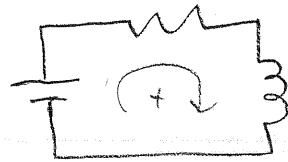

$$\text{KVL} \Rightarrow \varepsilon - iR - L \frac{di}{dt} = 0$$

$$\Rightarrow \frac{di}{dt} = \frac{\varepsilon}{L} - i \frac{R}{L}$$

$$\Rightarrow i(t) = \frac{\varepsilon}{R} (1 - e^{-tR/L})$$

$$C = \frac{Q}{V}$$

a)

$$i\left(\frac{1}{2} s\right) = \frac{50 \text{ V}}{25 \Omega} \left(1 - e^{-\frac{(0.5) s \cdot 25 \Omega}{10 \text{ mH}}}\right)$$

$\approx 0$

$$\approx \frac{50 \text{ V}}{25 \Omega}$$


$$U_L = \frac{1}{2} L I^2 = U_C = \frac{1}{2} \frac{Q^2}{C}$$

$$\Rightarrow \frac{Q^2}{C} = L I^2 \Rightarrow Q^2 = (LC) I^2 \Rightarrow Q = \sqrt{LC} I$$

$$\Rightarrow Q = \sqrt{10 \times 10^{-3} \text{ H} \cdot 20 \times 10^{-6} \text{ F}} \cdot \frac{50 \text{ V}}{25 \Omega} = \boxed{8.944 \times 10^{-4} \text{ C}}$$

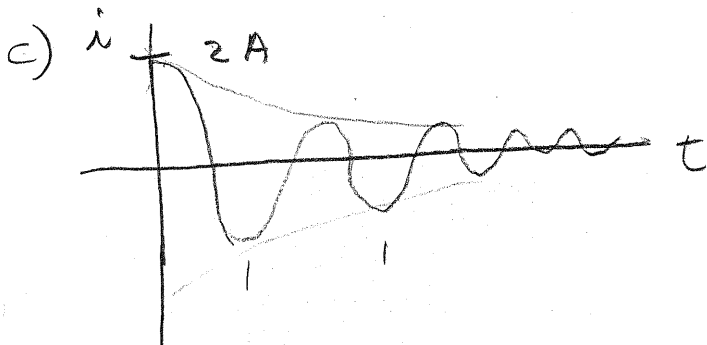b) ALL energy will go through the resistor  $r$ .

$$U = U_L = \frac{1}{2} L I^2 = \frac{1}{2} (10 \text{ mH}) \left(\frac{50 \text{ V}}{25 \Omega}\right)^2 = 20 \text{ mJ} = \boxed{0.02 \text{ J}}$$



30.69 In the circuit shown in Fig. 30.28,  $\mathcal{E} = 60.0 \text{ V}$ ,  $R_1 = 40.0 \Omega$ ,  $R_2 = 25.0 \Omega$ , and  $L = 0.300 \text{ H}$ . Switch S is closed at  $t = 0$ . Just after the switch is closed, a) What is the potential difference  $v_{ab}$  across the resistor  $R_1$ ? b) Which point, a or b, is at a higher potential? c) What is the potential difference  $v_{cd}$  across the inductor  $L$ ? d) Which point, c or d, is at a higher potential? The switch is left closed a long time and then opened. Just after the switch is opened, e) What is the potential difference  $v_{ab}$  across the resistor  $R_1$ ? f) Which point, a or b, is at a higher potential? g) What is the potential difference  $v_{cd}$  across the inductor  $L$ ? h) Which point, c or d, is at a higher potential?

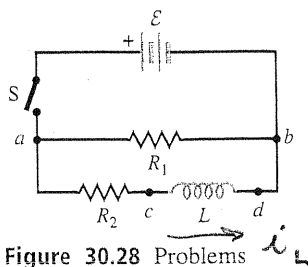


Figure 30.28 Problems 30.69, 30.70, and 30.75.

$t=0$  ~~switch~~ =  $\rightarrow$   $\leftarrow$

a) 60 volts


b) a

c)  $\mathcal{E} = 60 \text{ volts}$

d) c

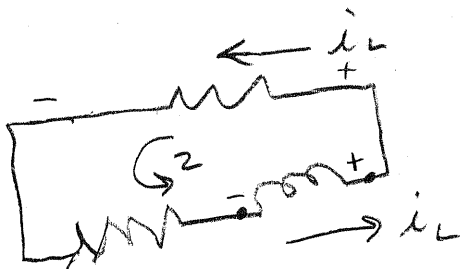e)  $i_L(t=\infty) = \frac{\mathcal{E}}{R_2} = \frac{60 \text{ V}}{25 \Omega} = 2.4 \text{ A}$

The current will be  $i_L(t=\infty) = 2.4 \text{ A}$



$\therefore V_{ab} = R_1 i_L = 40 \Omega (2.4 \text{ A}) = 96 \text{ volts}$

f) b from the direction of the current

g) KVL  $\textcircled{2} \Rightarrow -i_L R_1 - i_L R_2 - V_L = 0$

$\Rightarrow -V_L = i_L R_1 + i_L R_2 = (2.4 \text{ A})(40 \Omega + 25 \Omega)$   
= 156 volts

h) d

30.74 In the circuit shown in Fig. 30.31, neither the battery nor the inductors have any appreciable resistance, the capacitors are initially uncharged, and the switch S has been in position 1 for a very long time. Review the results of Problem 30.49. a) What is the current in the circuit?

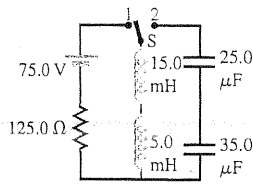



Figure 30.31 Problem 30.74.

a) The inductors act like a short.

$$\Rightarrow I = \frac{\mathcal{E}}{R} = \frac{75 \text{ V}}{125 \Omega}$$

$$= \boxed{0.6 \text{ A}}$$

b)

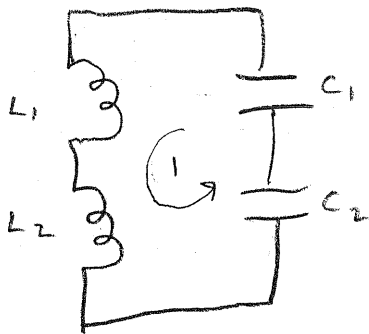

$$i(t=0) = 0.6 \text{ A}$$

$$\text{KVL} \Rightarrow -L_1 \frac{di}{dt} - L_2 \frac{di}{dt} - \frac{q}{C_1} - \frac{q}{C_2} = 0$$

$$\Rightarrow (L_1 + L_2) \frac{di}{dt} = - \left( \frac{C_1 + C_2}{C_1 C_2} \right) q$$

$$\Rightarrow \frac{d^2 q}{dt^2} = - \frac{C_1 + C_2}{C_1 C_2 (L_1 + L_2)} q$$

$\Rightarrow$  Simple Harmonic Motion


$$U_L = \frac{1}{2} L_{\text{eq}} i_{\text{max}}^2, \quad U_C = \frac{1}{2} \frac{Q^2}{C_{\text{eq}}}$$

Energy with switch from Capacitors to Inductors

$$U_L = U_C \Rightarrow Q^2 = C_{\text{eq}} L_{\text{eq}} i_{\text{max}}^2$$

$$Q = \sqrt{\frac{25(35)}{25+35} \times 10^{-6} \text{ F} (15+5) \times 10^{-3} \text{ H} (0.6 \text{ A})^2}$$
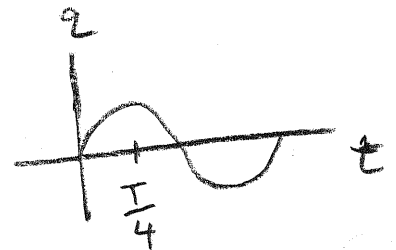
$$= \boxed{3.24037 \times 10^{-4} \text{ C}}$$



Time to charge will be  $\frac{1}{4}$  period of oscillation

$$= \frac{T}{4} = \frac{2\pi}{4\omega} = \frac{\pi}{2} \sqrt{LC} = \boxed{8.48 \times 10^{-4} \text{ s}}$$



30.77 Consider the circuit shown in Fig. 30.32. Switch S is closed at time  $t = 0$ , causing a current  $i_1$  through the inductive branch and a current  $i_2$  through the capacitive branch. The initial charge on the capacitor is zero, and the charge at time  $t$  is  $q_2$ .

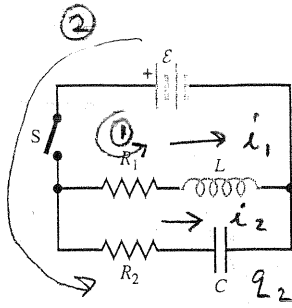


Figure 30.32 Challenge Problem 30.77.

a) Derive expressions for  $i_1$ ,  $i_2$ , and  $q_2$  as functions of time. Express your answers in terms of  $\mathcal{E}$ ,  $L$ ,  $C$ ,  $R_1$ ,  $R_2$ , and  $t$ . For the remainder of the problem let the circuit elements have the following values:  $\mathcal{E} = 48 \text{ V}$ ,  $L = 8.0 \text{ H}$ ,  $C = 20 \mu\text{F}$ ,  $R_1 = 25 \Omega$ , and  $R_2 = 5000 \Omega$ . b) What is the initial current through the inductive branch? What is the initial current through the capacitive branch? c) What are the currents through the inductive and capacitive branches a long time after the switch has been closed? How long is a "long time"? Explain. d) At what time  $t_1$  (accurate to two significant figures) will the currents  $i_1$  and  $i_2$  be equal? (Hint: You might consider using series expansions for the exponentials.) e) For the conditions given in part (d), determine  $i_1$ . f) The total current through the battery is  $i = i_1 + i_2$ . At what time  $t_2$  (accurate to two significant figures) will  $i$  equal one-half of its final value? (Hint: The numerical work is greatly simplified if one makes suitable approximations. A sketch of  $i_1$  and  $i_2$  versus  $t$  may help you decide what approximations are valid.)

$$\text{KVL } \textcircled{1} \Rightarrow \mathcal{E} - i_1 R_1 - L \frac{di_1}{dt} = 0$$

$$\text{KVL } \textcircled{2} \Rightarrow \mathcal{E} - i_2 R_2 - \frac{q_2}{C} = 0$$

The two loops act independent of each other, because  $\mathcal{E}$  is constant,

$$i_1(t) = \frac{\mathcal{E}}{R_1} (1 - e^{-t/R_1 L})$$

$$i_2(t) = \frac{\mathcal{E}}{R_2} e^{-t/R_2 C}$$

$$q_2(t) = \mathcal{E} C (1 - e^{-t/R_2 C})$$

$$\text{b) } i_1(t=0) = 0 \quad i_2(t=0) = \frac{\mathcal{E}}{R_2} = \frac{48 \text{ V}}{5000 \Omega} = 9.6 \text{ mA}$$

$$\text{c) } i_1(t=\infty) = \frac{\mathcal{E}}{R_1} = \frac{48 \text{ V}}{25 \Omega} = 1.92 \text{ A} \quad i_2(t=\infty) = 0$$

$$\tau_L = \frac{L}{R_1} = \frac{8 \text{ H}}{25 \Omega} = 0.32 \text{ s} \quad \tau_C = R_2 C = (5000 \Omega)(20 \times 10^{-6} \text{ F}) = 0.1 \text{ sec}$$

time  $\gg 0.32 \text{ s}$  is a long time

$$\text{d) } i_1(t_1) = i_2(t_1) \Rightarrow \frac{1 - e^{-t_1/R_1 L}}{R_1} = \frac{e^{-t_1/R_2 C}}{R_2} \quad e^{-x} \sim 1 - x$$

$$\Rightarrow \left[ 1 - \left( 1 - \frac{t_1 R_1}{L} \right) \right] R_2 \approx R_1 \left( 1 - \frac{t_1}{R_2 C} \right) \Rightarrow \frac{t_1 R_1 R_2}{R_1 L} = 1 - \frac{t_1}{R_2 C}$$

$$\Rightarrow t_1 \left( \frac{R_2}{L} + \frac{1}{R_2 C} \right) = 1 \Rightarrow t_1 = \frac{1}{\left( \frac{R_2}{L} + \frac{1}{R_2 C} \right)} = \frac{1}{\left( \frac{5000 \Omega}{8 \text{ H}} \right) + \frac{1}{5000 \Omega (20 \times 10^{-6})}}$$

$$\Rightarrow t_1 = \boxed{1.599744 \text{ ms}} \text{ this is small compared to } \frac{L}{R_1} \text{ and } R_1 C \text{ so it worked}$$

$$e) \quad i_1(t_1) = 1.92 \text{ A} \left( 1 - e^{-t_1/0.32 \text{ s}} \right)$$

$$t_1 = 0.001599744 \text{ s}$$


$$= \boxed{9.57 \times 10^{-3} \text{ A}}$$

$$i_2(t) = \frac{\mathcal{E}}{R_2} e^{-t/R_2} = 9.6 \text{ mA} e^{-\frac{0.0015997}{0.1}}$$

$$\approx 9.5 \times 10^{-3} \text{ A} \quad \checkmark$$

$$f) \quad i(t=\infty) = \frac{\mathcal{E}}{R_1}$$
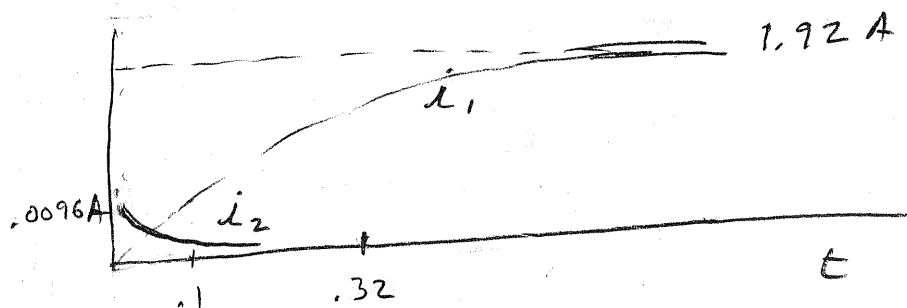
$$i(t_2) = \frac{\mathcal{E}}{2R_1} = \frac{\mathcal{E}}{R_1} \left( 1 - e^{-t_2 \frac{R_1}{L}} \right) + \frac{\mathcal{E}}{R_2} e^{-t_2/R_2}$$



$$i(t_2) \approx \frac{\mathcal{E}}{R_1} \left( 1 - e^{-t_2 \frac{R_1}{L}} \right) = \frac{\mathcal{E}}{2R_1}$$

$$\Rightarrow e^{-t_2 \frac{R_1}{L}} = \frac{1}{2} \Rightarrow \ln 2 = t_2 \frac{R_1}{L}$$

$$\Rightarrow t_2 = \frac{L}{R} \ln 2 = \frac{8 \text{ H}}{25 \Omega} \ln 2 \approx \boxed{0.222 \text{ s}}$$


31.1 The voltage across the terminals of an ac power supply varies with time according to Eq. (31.1). The voltage amplitude is  $V = 45.0 \text{ V}$ . What is a) the root-mean-square potential difference  $V_{\text{rms}}$ ? b) the average potential difference  $V_{\text{av}}$  between the two terminals of the power supply?

$$\text{Eq. (31.1)} \quad v = V \cos \omega t$$

$$\text{a)} \quad V_{\text{rms}} = \sqrt{\frac{1}{\left(\frac{2\pi}{\omega}\right)} \int_0^{t' = \frac{2\pi}{\omega}} V^2 \cos^2 \omega t \, dt} = \frac{V}{\sqrt{2}} = \frac{45 \text{ V}}{\sqrt{2}} = \boxed{31.82 \text{ V}}$$

$$\text{b)} \quad V_{\text{ave}} = \frac{1}{\left(\frac{2\pi}{\omega}\right)} \int_0^{t' = \frac{2\pi}{\omega}} V \cos \omega t \, dt = \boxed{0}$$

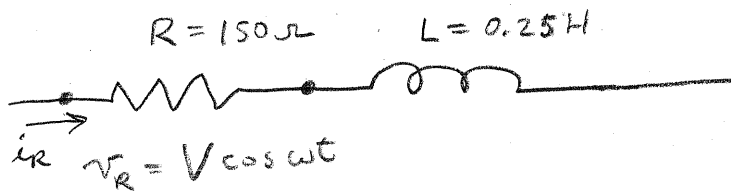31.9 A  $150\text{-}\Omega$  resistor is connected in series with a  $0.250\text{-H}$  inductor. The voltage across the resistor is  $v_R = (3.80\text{ V}) \cos [(720\text{ rad/s})t]$ . a) Derive an expression for the circuit current. b) Determine the inductive reactance of the inductor. c) Derive an expression for the voltage  $v_L$  across the inductor.



a)

$$i_R = \frac{v_R}{R} = \frac{V}{R} \cos \omega t = \frac{3.8\text{ V}}{150\ \Omega} \cos \omega t$$

$$= \boxed{0.025\bar{3}\text{ A} \cos\left(720\frac{\text{rad}}{\text{s}}t\right)}$$

b)

$$X_L = \omega L = \left(720\frac{\text{rad}}{\text{s}}\right)(0.25\text{ H}) = \boxed{180\ \Omega} \quad \angle 90^\circ \text{ Lead}$$

$v_L$  Leads  $i_L$

c)

$$v_L = I X_L = \left(\frac{3.8\text{ V}}{150\ \Omega}\right)(180\ \Omega) \cos(\omega t + 90^\circ)$$

$$= \boxed{-4.58\text{ V} \sin\left(720\frac{\text{rad}}{\text{s}}t\right)}$$

or

$$v_L = L \frac{di}{dt} = L \frac{d}{dt} \left( \frac{V}{R} \cos \omega t \right) = \frac{LV}{R} \omega (-\sin \omega t)$$

$$= -4.58\text{ V} \sin\left(720\frac{\text{rad}}{\text{s}}t\right)$$

