

31.18 31.17 $\pi w \ll$ 

31.18, 37, 38, 46, 52

$$d) v_R = IR = (0.04992 \text{ A})(200 \Omega) = \boxed{9.98 \text{ V}}$$

$$v_L = IX_L = (0.04992 \text{ A})\left(\frac{250}{s}\right)(0.1 \text{ H}) = \boxed{4.99 \text{ V} \angle 90^\circ \text{ Lead}}$$

$$v_C = IX_C = \frac{(0.04992 \text{ A})}{\left(\frac{250}{s}\right)(6 \times 10^{-6} \text{ F})} = \boxed{33.28 \text{ V} \angle 90^\circ \text{ Lag}}$$

e) Not in the same phase

31.18 from 31.17

$$a) i = I \cos \omega t \quad v = v_R(t) + v_L(t) + v_C(t)$$

$$v(t) = 30 \text{ V} \cos\left(\frac{250}{s}t - 70.56^\circ\right)$$

$$v_R(t) = 9.98 \text{ V} \cos\left(\frac{250}{s}t\right)$$


$$v_L = 4.99 \text{ V} \cos\left(\frac{250}{s}t + 90^\circ\right)$$

$$v_C = 33.28 \text{ V} \cos\left(\frac{250}{s}t - 90^\circ\right)$$

See over for plot

31.18 (continued)

(Volts)

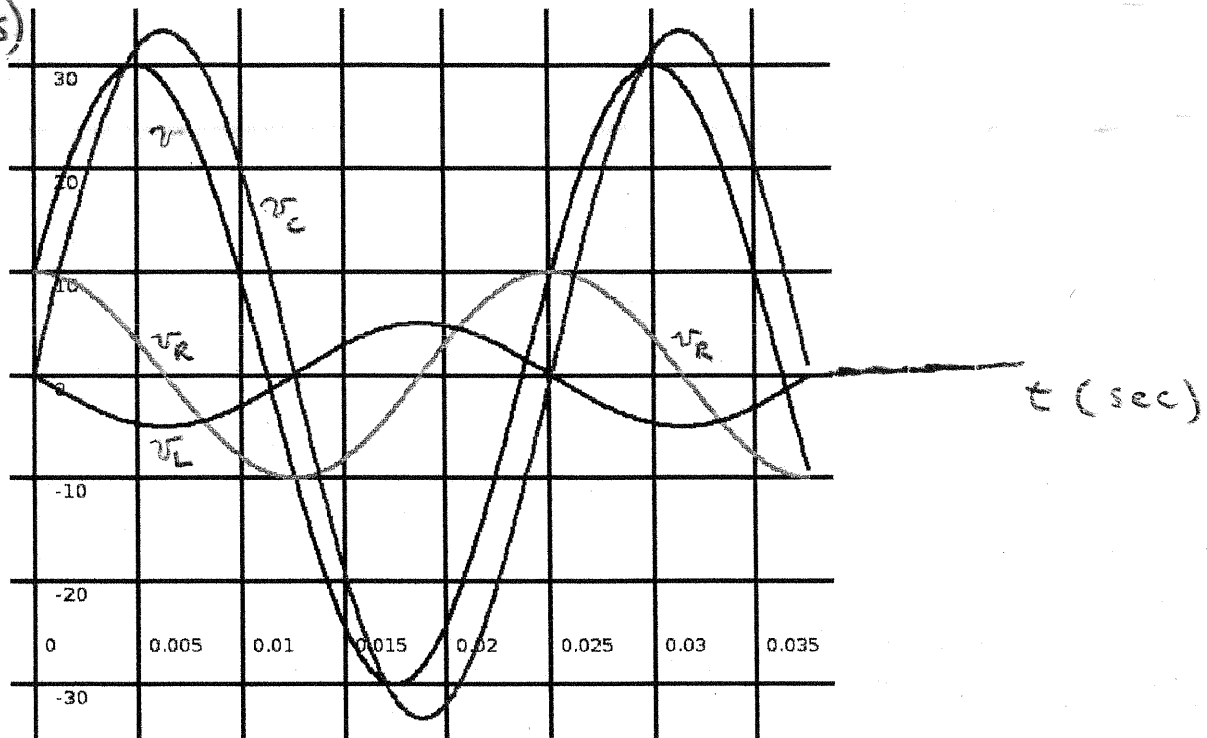

$$t = 20 \text{ ms}$$

$$t = 20 \text{ ms} = 0.025 \text{ s}$$

$$b) \quad v = -24.29 \text{ V}, \quad v_R = 2.83 \text{ V}, \quad v_L = 4.785 \text{ V}, \quad v_C = -31.91$$



$$v = v_R + v_L + v_C$$

$$c) \quad t = 40 \text{ ms} = 0.04 \text{ s}$$

$$v = 23.76 \text{ V}, \quad v_R = -8.37 \text{ V}, \quad v_L = 2.72 \text{ V}, \quad v_C = -18.1$$

$$v = v_R + v_L + v_C$$

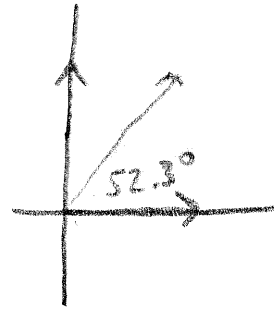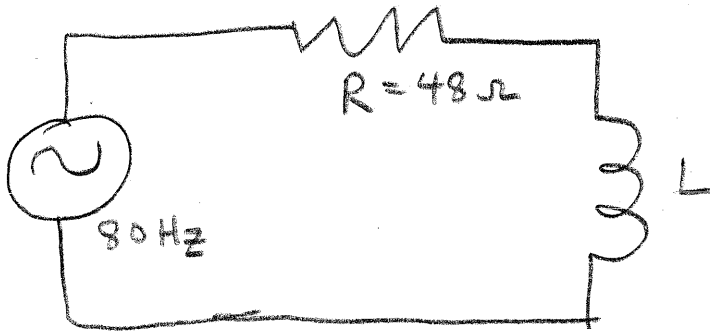
31.37 A coil has a resistance of  $48.0 \Omega$ . At a frequency of  $80.0 \text{ Hz}$  the voltage across the coil leads the current in it by  $52.3^\circ$ . Determine the inductance of the coil.



$$\tan \theta = \frac{X_L}{R} = \frac{L\omega}{R} \Rightarrow L = \frac{R}{\omega} \tan \theta$$

$$= \frac{48 \Omega}{80 \frac{1}{s} \left( \frac{2\pi \text{ rad}}{\text{cyc}} \right)} \tan 52.3^\circ = \boxed{0.1236 \text{ H}}$$

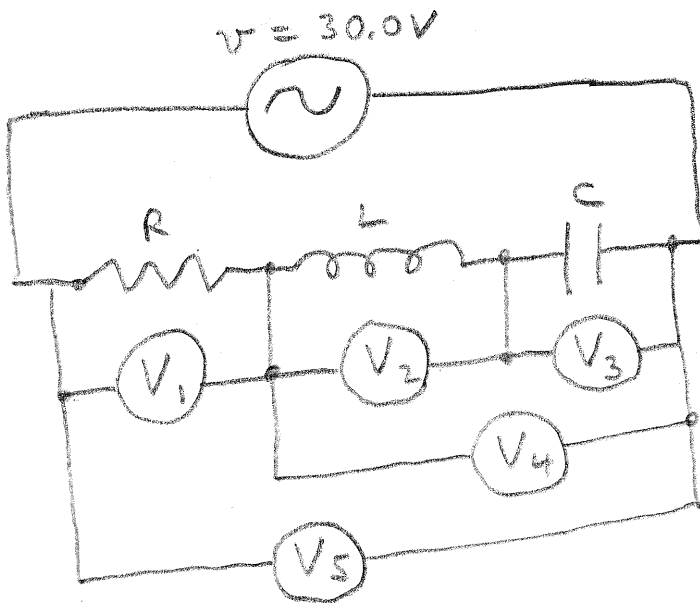31.38 Five infinite-impedance voltmeters, calibrated to read rms values, are connected as shown in Fig 31.21. Let  $R = 200 \Omega$ ,  $L = 0.400 \text{ H}$ ,  $C = 6.00 \mu\text{F}$ , and  $V = 30.0 \text{ V}$ . What is the reading of each voltmeter if a)  $\omega = 200 \text{ rad/s}$ ; b)  $\omega = 1000 \text{ rad/s}$ ?



$$X_L = \omega L = 80 \Omega$$

$$X_C = \frac{1}{\omega C} = 833.3 \Omega$$

$$R = 200 \Omega$$

$$a) \quad I = \frac{V}{Z} \quad Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$Z = \sqrt{(200 \Omega)^2 + \left(200 \frac{\text{rad}}{\text{s}} (0.4 \text{ H}) - \frac{1}{(200 \frac{\text{rad}}{\text{s}}) (6 \times 10^{-6} \text{ F})}\right)^2}$$

$$= 779.43 \Omega$$

$$I = \frac{V}{Z} = 0.0384897 \text{ A}$$

rms

$$V_1 = \frac{IR}{\sqrt{2}} = 5.44 \text{ V}$$

$$V_2 = \frac{IX_L}{\sqrt{2}} = 2.18 \text{ V}$$

$$V_3 = \frac{IX_C}{\sqrt{2}} = 22.68 \text{ V}$$

$$V_4 = \frac{I(X_C - X_L)}{\sqrt{2}} = 20.5 \text{ V}$$

$$V_5 = \frac{30}{\sqrt{2}} = 21.2 \text{ V}$$

$$31,38 \quad b) \quad \omega = 1000 \text{ rad/s}$$

$$X_L = \omega L = 400 \Omega \quad X_C = 166,6 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 307,3 \Omega$$

$$I = \frac{V}{Z} = 0,0976187 \text{ A}$$

$$V_1 = \frac{IR}{\sqrt{2}} = 13,8 \text{ V} \quad V_2 = \frac{IX_L}{\sqrt{2}} = 27,6 \text{ V}$$

$$V_3 = \frac{IX_C}{\sqrt{2}} = 11,5 \text{ V} \quad V_4 = \frac{|IX_C - IX_L|}{\sqrt{2}} = 16,1 \text{ V}$$

$$V_5 = \frac{30 \text{ V}}{\sqrt{2}} = 21,2 \text{ V}$$

**31.46 A Low-Pass Filter.** Figure 31.23 shows a low-pass filter (see Problem 31.45); the output voltage is taken across the capacitor in an  $L$ - $R$ - $C$  series circuit. Derive an expression for  $V_{out}/V_s$ , the ratio of the output and source voltage amplitudes, as a function of the angular frequency  $\omega$  of the source. Show that when  $\omega$  is large this ratio is proportional to  $\omega^{-2}$  and thus is very small, and show that the ratio approaches unity in the limit of small frequency.

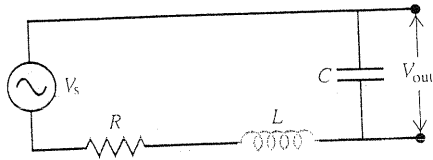


Figure 31.23 Problem 31.46.

$$a) \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$I = \frac{V_s}{Z} \quad V_{out} = I X_C = \frac{V_s}{Z} X_C = \frac{V_s \frac{1}{\omega C}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\Rightarrow \frac{V_{out}}{V_s} = \frac{1}{\omega C} \left[ R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \right]^{-1/2}$$

for  $\omega$  large

$$\frac{V_{out}}{V_s} = \frac{1}{\omega C} \frac{1}{\omega L} \frac{1}{\sqrt{\left(\frac{R}{\omega L}\right)^2 + \left(1 - \frac{1}{\omega^2 LC}\right)^2}}$$

$$\Rightarrow \frac{V_{out}}{V_s} = \frac{1}{\omega^2 LC} \frac{1}{\sqrt{\underbrace{\left(\frac{R}{\omega L}\right)^2}_{\text{small}} + \left[1 - \underbrace{\left(\frac{1}{\omega^2 LC}\right)}_{\text{small}}\right]^2}} \approx \frac{1}{\omega^2} \frac{1}{LC} \frac{1}{\sqrt{1}}$$

$$\omega L \gg R$$


$$\omega^2 \gg \frac{1}{LC}$$

$$\Rightarrow \frac{V_{out}}{V_s} \propto \frac{1}{\omega^2}$$

for small  $\omega$

$$\frac{V_{out}}{V_s} = \frac{1}{\omega C} \frac{1}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{\underbrace{R^2 \omega^2 C^2}_{\text{small}} + \underbrace{\left(\omega^2 LC - 1\right)^2}_{\text{small}}}} \approx 1$$

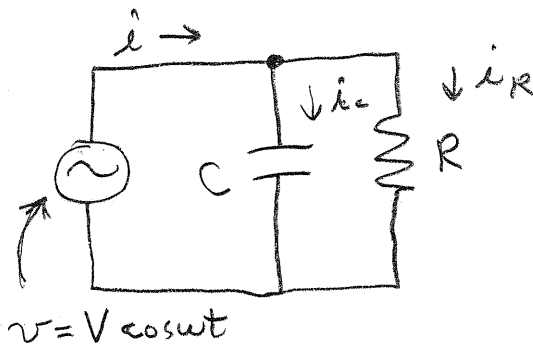
31.52 A 400-Ω resistor and a 6.00-μF capacitor are connected in parallel to an ac generator that supplies an rms voltage of 220 V at an angular frequency of 360 rad/s. Use the results of Problem 31.50. Note that since there is no inductor in the circuit, the  $1/\omega L$  term is not present in the expression for Z. Find a) the current amplitude in the resistor; b) the current amplitude in the capacitor; c) the phase angle of the source current with respect to the source voltage; d) the amplitude of the current through the generator. e) Does the source current lag or lead the source voltage?



$$KCR \Rightarrow i = i_c + i_R = C \frac{dv}{dt} + \frac{v}{R}$$

$$\Rightarrow i = -C \omega V \sin \omega t + \frac{V \cos \omega t}{R}$$
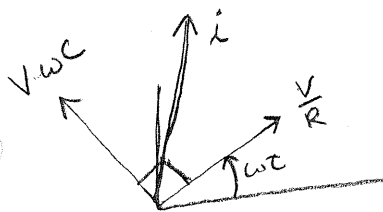
$$\begin{aligned} \Rightarrow i &\equiv I \cos(\omega t + \phi) = -\omega C V \sin \omega t + \frac{V}{R} \cos \omega t \\ &= \omega C V \cos(\omega t + 90^\circ) + \frac{V}{R} \cos \omega t \end{aligned}$$



$$i = \sqrt{\underbrace{(\omega C V)^2}_{I_c^2} + \underbrace{\left(\frac{V}{R}\right)^2}_{I_R^2}}$$

$I$

$$\cos \left[ \omega t + \tan^{-1} \left( \frac{\omega C}{\frac{1}{R}} \right) \right]$$

$$\tan \phi = \frac{\omega C V}{\frac{V}{R}} = \frac{I_c}{I_R}$$

a)

$$\Rightarrow I_R = \frac{V}{R} = \frac{\sqrt{2} (220 \text{ V})}{400 \Omega} = \boxed{0.778 \text{ A}}$$


b)

$$i_c = \omega C V \sin \omega t \Rightarrow I_c = \omega C V = (360 \frac{\text{rad}}{\text{s}})(6 \times 10^{-6} \text{ F})(\sqrt{2})(220 \text{ V})$$

$$I_c = \boxed{0.672 \text{ A}}$$

c)
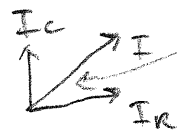
$$\phi = \tan^{-1} \left( \frac{\omega C}{\frac{1}{R}} \right) = \tan^{-1} \left( (360)(6 \times 10^{-6})(400) \right) = \boxed{40.8^\circ}$$



$$d) I = \sqrt{I_c^2 + I_R^2} = \boxed{1.03 A}$$

e)  $\hat{i}$  leads  $v$